

Electricity Lab. Experiment No. (6)

# Determination of Resistance of Resistors in Series and in

## **Parallel in Simple Circuit**

## **1. Introduction**

You know that every material offers some resistance to the flow of current. If we have two or more resistances in an electrical circuit, can we find out the equivalent of these resistances? Theoretically, you must have learnt answer to this question in your school physics course. In this experiment, you will verify the law of combination of resistances. Let us discuss the theory used in this experiment briefly.

## 2. Theory

Consider an electrical conductor. Let V is the voltage and I is the current flowing through the conductor. Then the ratio of V and I is equal to a quantity which is a measure of the resistance offered by the conductor to the flow of charge. There is a relationship between these parameters V, I and R which is known as Ohm's law. Simple circuits can be used to demonstrate Ohm's law. This law states that

$$\frac{V}{I} = R \tag{1}$$

where R is the resistance. Resistors can be connected in two ways. The resistance R can be net resistance of two or more resistors which are either in series, (that is connected end to end) or in parallel (that is connected to the same two points) as shown in Fig. 6.1(a) and Fig. 6.1(b) respectively.



Fig. 1 (b) Resistors in Parallel

Al-Karkh University of Science College of Science Medical Physics Department



Electricity Lab. Experiment No. (6)

If there are two or more than two resistors in any given circuit, it is always possible to replace a combination of resistors with a single resistor and leave unchanged the potential differences between the terminals of combination and current in the rest of the circuit. This single resistance is called the *equivalent resistance*. In this experiment, two resistors  $R_1$  and  $R_2$  will be used. They will be joined in series and in parallel while the potential V and the current I will be varied. If the resistors are connected in series (as shown in Fig. 1.a), then the equivalent resistance of  $R_1$  and  $R_2$  is given by the relation

$$R_S = R_1 + R_2 \tag{2}$$

The equivalent resistance of  $R_1$  and  $R_2$  connected in parallel (as shown in Fig. 1.b) is given by the relation

$$\frac{1}{R_{P}} = \frac{1}{R_{1}} + \frac{1}{R_{2}}$$
$$\frac{1}{R_{P}} = \frac{R_{1} + R_{2}}{R_{1}R_{2}}$$
$$R_{P} = \frac{R_{1}R_{2}}{R_{1} + R_{2}}$$
(3)

#### **3. AIMS AND OBJECTIVES**

Aims of this experiment are to:

- practically verify the law of combination of resistances in series;
- practically verify the law of combination of resistances in parallel;
- apply Ohm's law by means of drawing appropriate graph to obtain values of net resistances in a simple circuit.

## 4. Procedure

- 1. Identify all apparatus.
- 2. Connect the circuit as shown in Fig. 3. with  $R_1$  and  $R_2$  in series.
- 3. Make all connections tight.
- 4. Adjust the Rheostat ( $R_h$ ) and obtain a series of six readings of current  $I_1$  and voltage  $V_1$  from the Ammeter and Voltmeter respectively.
- 5. Now connect  $R_1$  and  $R_2$  in parallel.
- 6. Repeat the steps 3 and 4 to obtain six new sets of values of current  $I_1$  and voltage  $V_1$ .
- 7. Record the readings for both cases in Table 1.

Al-Karkh University of Science College of Science Medical Physics Department



Electricity Lab. Experiment No. (6)



Fig. 3

#### 4.1 Data Analysis

Table 1.: The values of current and voltages

	When resistance $R_1$ and $R_2$		When resistance R <sub>1</sub> and R <sub>2</sub>	
S.No.	in Series		in Parallel	
	V <sub>1</sub>	I <sub>1</sub>	$V_2$	$I_2$
1.				
2.				
3.				
4.				
5.				
6.				

- Plot a graph of  $V_1$  versus  $I_1$  using the data set collected in the Table 1, when resistors are in series.
- Similarly a second graph can be plotted between V<sub>2</sub> versus I<sub>2</sub> using the data set collected in Table 1 when the resistors are in parallel.
- From these graphs, obtain the slopes S<sub>1</sub> and S<sub>2</sub>.
- These slopes give the values of resistances in series and in parallel according to:

$$slope = \frac{\Delta I}{\Delta V}$$
$$R = \frac{1}{Slope}$$

## 4.2 RESULT

- The value of resistance in series combination is.....
- The value of resistance in parallel combination is ......

#### **5. CONCLUSION**

- a) What do the slopes S1 and S2 represent?
- b) Compare the slopes S1 and S2 with the values of R obtained using Eqs. 2 and 3 respectively.
- c) What are the accuracies of the values of the resistors for the two circuits obtained?
- d) What conclusions can you draw from this experiment?